

Block Diagram

Meg McCauley

High Level Walk Through

Button checking occurs every clock cycle

User pushes button, debouncing occurs, system says button = on


Set state counter to state counter + 1

Set LED state to corresponding state counter

Repeat

Four Important Pieces

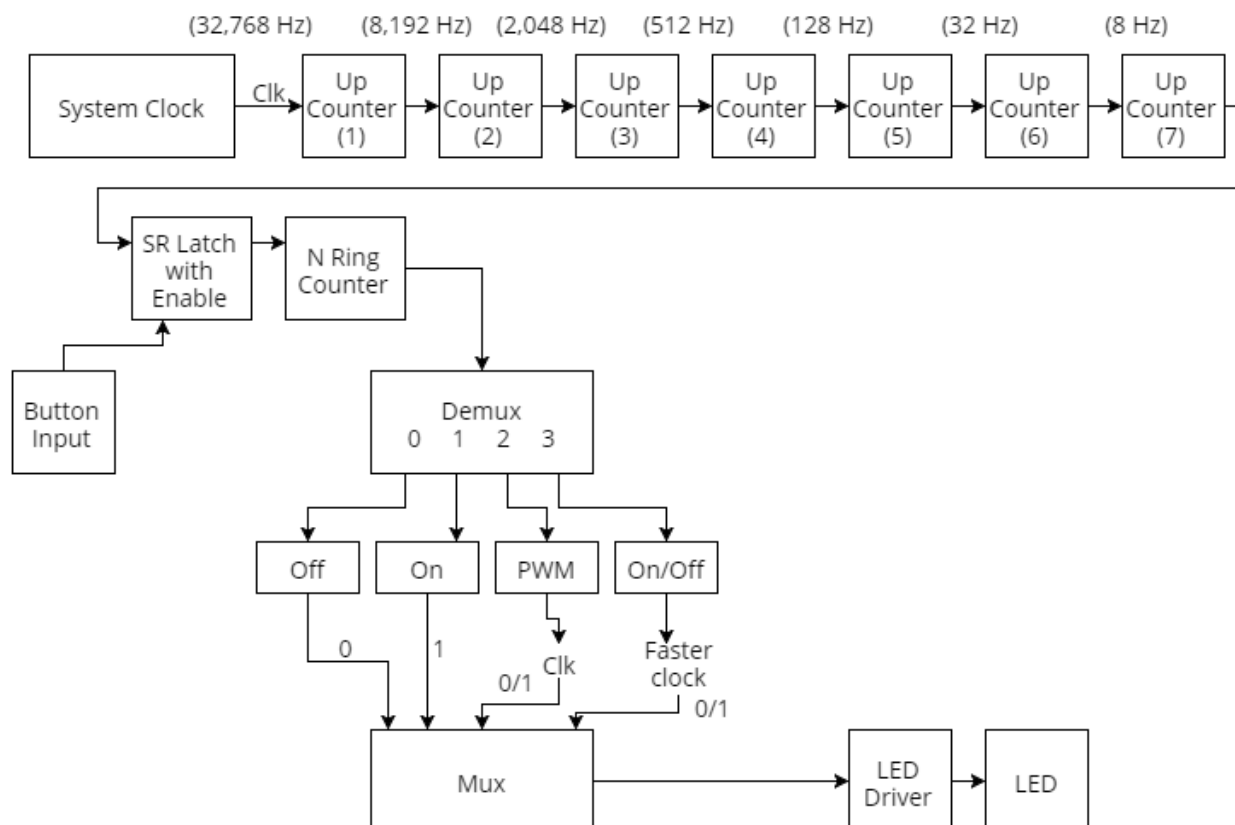1. Timing
2. Button Push
3. State Select
4. LED Driving



External Resources

Up Counters: <http://www.allaboutcircuits.com/textbook/digital/chpt-11/synchronous-counters/>

Input Conditioning: <https://www.acromag.com/page/signal-conditioning>

Debouncing: <http://www.ganssle.com/debouncing-pt2.htm>